

The City College of New York  
Computer Organization Lab  
**CSC 34300**  
(Spring 2024)

**LAB 4**  
**8 Bit Shift\_ADD\_Multiplier**

**Mahir Asef**

**Instructor: Albi Arapi**

**Date: 04.18.2024**

## **Table of Contents**

**Objective -----Page 3**

**Functionality and Specifications-----Page 3**

**Simulation-----Page 11**

**Conclusion-----Page 12**

## Objective:

The purpose of this lab experiment is to introduce ourselves to working with add shift multiplier in Quartus. By the end of this experiment, we will be able to understand how the add shift multiplier operates on multiplier and multiplicands as well as how it stores the product at each iteration in the product register. We will learn how to create the components necessary to create an 8 bit add shift multiplier by using D flip flop, full adder, ripple carry adder etc. Throughout the experiment, we will be replicating VHDL code for each component part and then connect them together to build the entire design of the add shift multiplier. We will also do a design verification using modelSim at the end to demonstrate the functionality of our circuit for which we will also replicate testbench code.

## Functionality and Specifications:

### Controller:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  entity Controller is
6  port (reset : in std_logic ;
7        clk : in std_logic ;
8        START : in std_logic ;
9        LSB : in std_logic ;
10       ADD_cmd : out std_logic ;
11       SHIFT_cmd : out std_logic ;
12       LOAD_cmd : out std_logic ;
13       STOP : out std_logic);
14  end;
15  architecture rtl of Controller is
16  signal temp_count : std_logic_vector(2 downto 0);
17  -- declare states
18  type state_typ is (IDLE, INIT, TEST, ADD, SHIFT);
19  signal state : state_typ;
20  begin
21  process (clk, reset)
22  begin
23  if reset='0' then
24  state <= IDLE;
25  temp_count <= "000";
26  elsif (clk'event and clk='1') then
27  case state is
28  when IDLE =>
29  if START = '1' then
30  state <= INIT;
31  else
32  state <= IDLE;
33  end if;
34  when INIT =>
35  state <= TEST;
36  when TEST =>
37  if LSB = '0' then
38  state <= SHIFT;
39  else
40  state <= ADD;
41  end if;
42  when ADD =>
43  state <= SHIFT;
44  when SHIFT =>
45  if temp_count = "111" then -- verify if finished

```

```

46 temp_count <= "000"; -- re-initialize counter
47 state <= IDLE; -- ready for next multiply
48 else
49 temp_count <= temp_count + 1; -- increment counter
50 state <= TEST;
51 end if;
52 end case;
53 end if;
54 end process;
55 STOP <= '1' when state = IDLE else '0';
56 ADD_cmd <= '1' when state = ADD else '0';
57 SHIFT_cmd <= '1' when state = SHIFT else '0';
58 LOAD_cmd <= '1' when state = INIT else '0';
59 end rtl;

```

#### D Flip Flop:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity DFF is
4  port (reset : in std_logic ;
5        clk : in std_logic ;
6        D : in std_logic ;
7        Q : out std_logic);
8  end;
9  architecture behav of DFF is
10 begin
11 process (clk, reset)
12 begin
13 if reset='0' then
14 Q <= '0'; -- clear register
15 elsif (clk'event and clk='1') then
16 Q <= D; -- load register
17 end if;
18 end process;
19 end behav;
20

```

**Multiplicand:**

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity Multiplicand is
4  port (reset : in std_logic ;
5        A_in : in std_logic_vector (7 downto 0);
6        LOAD_cmd : in std_logic ;
7        RA : out std_logic_vector (7 downto 0));
8  end;
9  architecture struc of Multiplicand is
10 component DFF
11 port (
12   reset : in std_logic;
13   clk : in std_logic;
14   D : in std_logic;
15   Q : out std_logic
16 );
17 end component;
18 begin
19 DFFs: for i in 7 downto 0 generate
20   DFFReg:DFF port map (reset, LOAD_cmd, A_in(i), RA(i));
21 end generate;
22 end struc;

```

**Multiplier:**

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity Multiplier_Result is
4  port (reset : in std_logic ;
5        clk : in std_logic ;
6        B_in : in std_logic_vector (7 downto 0);
7        LOAD_cmd : in std_logic ;
8        SHIFT_cmd : in std_logic ;
9        ADD_cmd : in std_logic ;
10 Add_out : in std_logic_vector (7 downto 0);
11 C_out : in std_logic ;
12 RC : out std_logic_vector (15 downto 0);
13 LSB : out std_logic ;
14 RB : out std_logic_vector (7 downto 0));
15 end;
16 architecture rtl of Multiplier_Result is
17   signal temp_register : std_logic_vector(16 downto 0);
18   signal temp_Add : std_logic;
19 begin
20 process (clk, reset)
21 begin
22   if reset='0' then
23     temp_register <= (others => '0'); -- initialize temporary register
24     temp_Add <= '0';
25   elsif (clk'event and clk='1') then
26     if LOAD_cmd = '1' then
27       temp_register(16 downto 8) <= (others => '0');
28       temp_register(7 downto 0) <= B_in; -- load B_in into register
29     end if;
30     if ADD_cmd = '1' then
31       temp_Add <= '1';
32     end if;
33     if SHIFT_cmd = '1' then
34       if temp_Add = '1' then
35         -- store adder output while shifting register right 1 bit
36         temp_Add <= '0';
37         temp_register <= '0' & C_out & Add_out & temp_register (7 downto 1);

```

```

38 else
39 -- no add - simply shift right 1 bit
40 temp_register <= '0' & temp_register (16 downto 1);
41 end if;
42 end if;
43 end if;
44 end process;
45 RB <= temp_register(15 downto 8);
46 LSB <= temp_register(0);
47 RC <= temp_register(15 downto 0);
48 end rtl;

```

### Full Adder:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity Full_Adder is
4  port (X : in std_logic;
5        Y : in std_logic;
6        C_in : in std_logic;
7        Sum : out std_logic;
8        C_out : out std_logic);
9  end;
10 architecture struc of Full_Adder is
11 begin
12 Sum <= X xor Y xor C_in;
13 C_out <= (X and Y) or (X and C_in) or (Y and C_in);
14 end struc;
15

```

### Ripple Carry Adder:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity RCA is
4  port (RA : in std_logic_vector (7 downto 0);
5        RB : in std_logic_vector (7 downto 0);
6        C_out : out std_logic;
7        Add_out : out std_logic_vector (7 downto 0));
8  end;
9  architecture struc of RCA is
10 signal c_temp : std_logic_vector(7 downto 0);
11 component Full_Adder
12 port (
13 X : in std_logic;
14 Y : in std_logic;
15 C_in : in std_logic;
16 Sum : out std_logic;
17 C_out : out std_logic;
18 );
19 end component;
20 begin
21 c_temp(0) <= '0'; -- carry in of RCA is 0
22 Adders: for i in 7 downto 0 generate
23 -- assemble first 7 adders from 0 to 6
24 Low: if i/=7 generate
25 FA:Full_Adder port map (RA(i), RB(i), c_temp(i), Add_out(i), c_temp(i+1));
26 end generate;
27 -- assemble last adder
28 High: if i=7 generate
29 FA:Full_Adder port map (RA(7), RB(7), c_temp(i), Add_out(7), C_out);
30 end generate;
31 end generate;
32 end struc;
33

```



## 8 Bit Add Shift Multiplier:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  --library synplify; -- required for synthesis
4  --use synplify.attributes.all; -- required for synthesis
5  entity Multiplier is
6  port (
7      A_in : in std_logic_vector(7 downto 0 );
8      B_in : in std_logic_vector(7 downto 0 );
9      clk : in std_logic;
10     reset : in std_logic;
11     START : in std_logic;
12     RC : out std_logic_vector(15 downto 0 );
13     STOP : out std_logic);
14 end Multiplier;
15 use work.all;
16 architecture rtl of Multiplier is
17     signal ADD_cmd : std_logic;
18     signal Add_out : std_logic_vector(7 downto 0 );
19     signal C_out : std_logic;
20     signal LOAD_cmd : std_logic;
21     signal LSB : std_logic;
22     signal RA : std_logic_vector(7 downto 0 );
23     signal RB : std_logic_vector(7 downto 0 );
24     signal SHIFT_cmd : std_logic;
25     component RCA
26     port (
27         RA : in std_logic_vector(7 downto 0 );
28         RB : in std_logic_vector(7 downto 0 );
29         C_out : out std_logic;
30         Add_out : out std_logic_vector(7 downto 0 )
31     );
32 end component;
33 component Controller
34 port (
35     reset : in std_logic;
36     clk : in std_logic;
37     START : in std_logic;
38     LSB : in std_logic;
39     ADD_cmd : out std_logic;
40     SHIFT_cmd : out std_logic;
41     LOAD_cmd : out std_logic;
42     STOP : out std_logic
43 );
44 end component;
45 component Multiplicand

```

```

46 port (
47     reset : in std_logic;
48     A_in : in std_logic_vector(7 downto 0 );
49     LOAD_cmd : in std_logic;
50     RA : out std_logic_vector(7 downto 0 )
51 );
52 end component;
53 component Multiplier_Result
54 port (
55     reset : in std_logic;
56     clk : in std_logic;
57     B_in : in std_logic_vector(7 downto 0 );
58     LOAD_cmd : in std_logic;
59     SHIFT_cmd : in std_logic;
60     ADD_cmd : in std_logic;
61     Add_out : in std_logic_vector(7 downto 0 );
62     C_out : in std_logic;
63     RC : out std_logic_vector(15 downto 0 );
64     LSB : out std_logic;
65     RB : out std_logic_vector(7 downto 0 )
66 );
67 end component;
68 begin
69     inst_RCA: RCA
70 port map (
71     RA => RA(7 downto 0),
72     RB => RB(7 downto 0),
73     C_out => C_out,
74     Add_out => Add_out(7 downto 0)
75 );
76     inst_Controller: Controller
77 port map (
78     reset => reset,
79     clk => clk,
80     START => START,
81     LSB => LSB,
82     ADD_cmd => ADD_cmd,
83     SHIFT_cmd => SHIFT_cmd,
84     LOAD_cmd => LOAD_cmd,
85     STOP => STOP
86 );
87     inst_Multiplicand: Multiplicand
88 port map (
89     reset => reset,
90     A_in => A_in(7 downto 0),

```



```

91 | LOAD_cmd => LOAD_cmd,
92 | RA => RA(7 downto 0)
93 | -);
94 | inst_Multiplier_Result: Multiplier_Result
95 | port map (
96 |   reset => reset,
97 |   clk => clk,
98 |   B_in => B_in(7 downto 0),
99 |   LOAD_cmd => LOAD_cmd,
100 |   SHIFT_cmd => SHIFT_cmd,
101 |   ADD_cmd => ADD_cmd,
102 |   Add_out => Add_out(7 downto 0),
103 |   C_out => C_out,
104 |   RC => RC(15 downto 0),
105 |   LSB => LSB,
106 |   RB => RB(7 downto 0)
107 | -);
108 | end rtl;
109

```

This is our full VHDL code for the 8 bits add shift multiplier. It's built by using controller component as well as a multiplicand component (A\_in) for the 8-bit multiplicand input and a multiplier component (B\_in) for the multiplier input which is also 8 bits. Multiplicand component is built from DFF. In addition, the design also a Full adder as well as a ripple carry adder. The add shift multiplier stores the product result in a 16-bit register named RC.

### Testbench Code:

```

1 | library ieee;
2 | use ieee.std_logic_1164.all;
3 | use ieee.numeric_std.all;
4 | use std.textio.all; --required for file I/O
5 | use ieee.std_logic_textio.all; --required for file I/O
6 | entity TESTBENCH is
7 |   end TESTBENCH;
8 | architecture BEHAVIORAL of TESTBENCH is
9 |   component Multiplier
10 |     port (
11 |       A_in : in std_logic_vector(7 downto 0 );
12 |       B_in : in std_logic_vector(7 downto 0 );
13 |       clk : in std_logic;
14 |       RC : out std_logic_vector(15 downto 0 );
15 |       reset : in std_logic;
16 |       START : in std_logic;
17 |       STOP : out std_logic
18 |     );
19 |   end component;
20 |   signal A_in_TB, B_in_TB : std_logic_vector(7 downto 0 );
21 |   signal clk_TB, reset_TB, START_TB : std_logic;
22 |   signal STOP_TB : std_logic;
23 |   signal RC_TB: std_logic_vector(15 downto 0);
24 |   begin
25 |     -- instantiate the Device Under Test
26 |     inst_DUT : Multiplier
27 |     port map (
28 |       A_in => A_in_TB,
29 |       B_in => B_in_TB,
30 |       clk => clk_TB,
31 |       reset => reset_TB,
32 |       RC => RC_TB,
33 |       START => START_TB,
34 |       STOP => STOP_TB);
35 |     -- Generate clock stimulus
36 |     STIMULUS_CLK : process
37 |     begin
38 |       clk_TB <= '0';
39 |       wait for 10 ns;
40 |       clk_TB <= '1';
41 |       wait for 10 ns;
42 |     end process STIMULUS_CLK;
43 |     -- Generate reset stimulus
44 |     STIMULUS_RST : process
45 |     begin

```


```

46 reset_TB <= '0';
47 wait for 50 ns;
48 reset_TB <= '1';
49 wait;
50 end process STIMULUS_RST;
51 -- Generate multiplication requests
52 STIMULUS_START : process
53 file logFile : text is out "bus_log.txt"; -- set output file name
54 variable L: line;
55 variable A_temp, B_temp, i : integer;
56 begin
57 write(L, string'("A B Result")); -- include heading in file
58 writeline(logFile,L);
59 A_temp := 0; -- start A at 0
60 B_temp := 255; -- start B at 255
61 i := 1;
62 for i in 1 to 256 loop
63 A_in_TB <= STD_LOGIC_VECTOR(to_unsigned(A_temp,8));
64 B_in_TB <= STD_LOGIC_VECTOR(to_unsigned(B_temp,8));
65 START_TB <= '0';
66 wait for 100 ns;
67 START_TB <= '1'; -- request the multiplier to start
68 wait for 100 ns;
69 START_TB <= '0';
70 wait until STOP_TB = '1'; -- wait for the multiplier to finish
71 hwrite(L, A_in_TB); -- insert hex value of A in file
72 write(L, string'(" "));
73 hwrite(L, B_in_TB); -- insert hex value of B in file
74 write(L, string'(" "));
75 hwrite(L, RC_TB); -- insert hex value of result in file
76 writeline(logFile,L);
77 A_temp := A_temp + 1; -- increment value of A (Multiplicand)
78 B_temp := B_temp - 1; -- decrement value of B (Multiplier)
79 end loop;
80 wait;
81 end process STIMULUS_START;
82 end BEHAVIORAL;
83


```

This is the testbench code that tests the add shift multiplier in modelsim in a work library. After simulation has been done the output register that stores product and the inputs multiplier and multiplicand will be saved in a text file called “bus\_log.txt”.

## Simulation:

 

This is the modelsim simulation of our circuit design. Here we have ran our simulation for 8000ns for a more zoomed in view to see how the multiplier value and multiplicand values changes. As we roll fro left to right, we can see that when multiplier bit is 1, the multiplicand value get added to the product register value. In the meantime multiplicand register shift 1 bit to the left while the multiplier register shifts 1 bit to the right and this process starts over and over again until the multiplier value is all 0 at each bit (in this case 00000000).

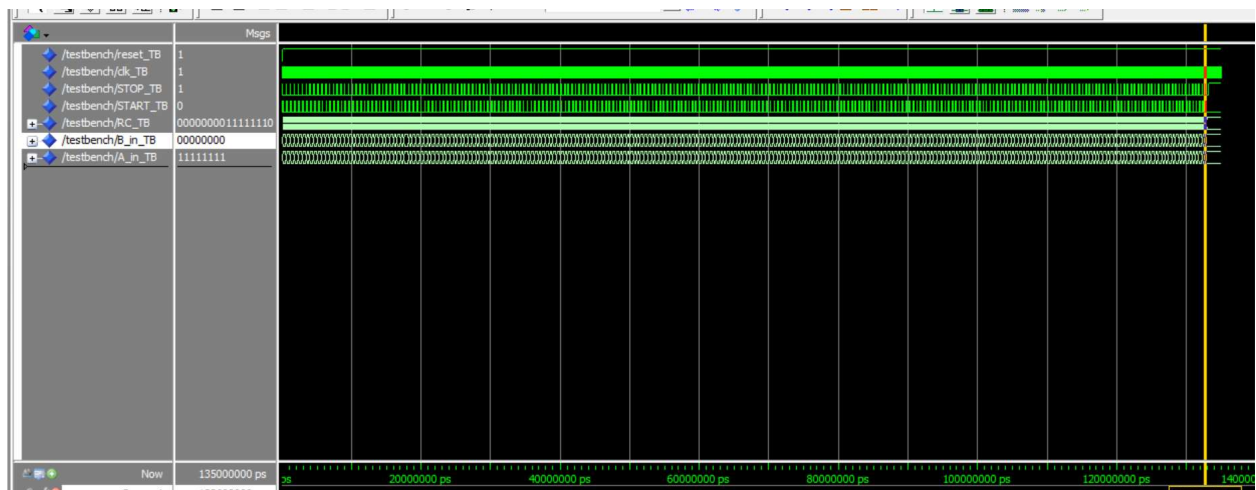

This simulation demonstartes the full process of 8 bit shift add multiplier which starts with the muliplier being set to 1111111 and multiplicand being set to 00000000. We run this simulation for 133000 ns and as we can see once it ends, all the multiplier values shift to the right making it 00000000 and all the multiplicand values shift to the left making it 11111111. This whole process lasts for 256 cycles since we are working with a 8 bit add shift multiplier.

## Conclusion:

We have reached the end of this laboratory experiment. Throughout this experiment, we were able to correctly understand and explain what an add shift multiplier is and define the functionality of an add shift multiplier as well as understanding how they store data or operate on data. Then we have started building our circuit that consists of connecting different components together. As shown above, we were able successfully create a controller, a DFF, a multiplier and a multiplicand a full adder and a ripple carry adder component and we have connected all of this together to build our add shift multiplier circuit. We were also able to successfully replicate a testbench code for simulation verification on modelsim. We have ran two different modelsim simulations to show the functionality and process by rolling through our simulation and explaining how the values changes and get stored in the output as demonstrated above. Overall, this lab has been very informative on learning about the design implementation of a 8 bit add shift multiplier which will allow us to build even more enhanced multiplier in future as well as expanding our knowledge on the realm of data storage and data process in hardware memory.